

get I_{OL2} because $M_1 \equiv M_2 \equiv M_3 \equiv M_4$

2014 Oct 11 W19700 d16




on 9th May 2010 VDD

VDD

no sym

, with
current mirror

id.

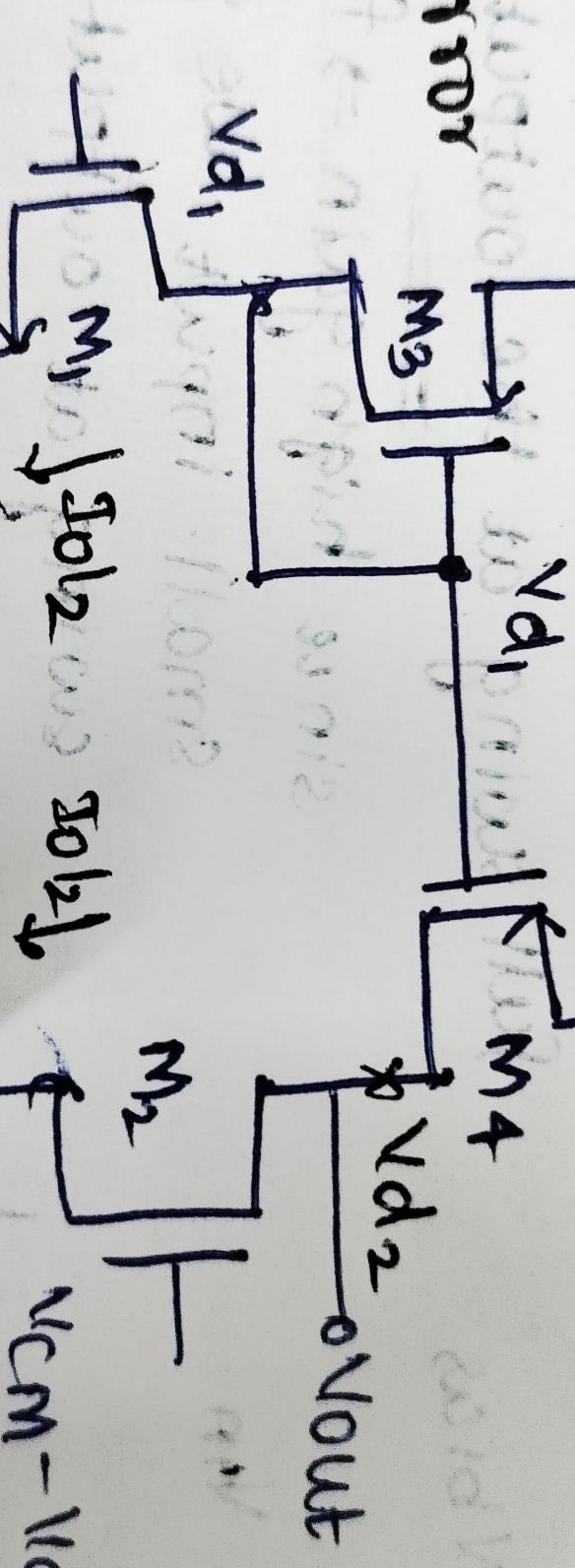

$V_{d1} = V_{d2}$

$$V_{CM} - \frac{V_d}{2}$$

$$V_{CM} + \frac{V_d}{2}$$

$\frac{V_d}{2}$ at midnode

$$\frac{V_d}{2}$$

M_1, M_2, M_3, M_4
all same length and
same some

$V_{SG1} = V_{SG2}$

$I_D = I_{OL1} = I_{OL2}$

Suppose $V_{d_2} = V_{d_1} + \Delta V$.

Assume channel length modulation.

$$so \ compare M_1 \& M_2 \Rightarrow (I_D)_{M_2} > (I_D)_{M_1}$$

In PMOS

because of V_{d_2} , M_3 current $> M_4$. ($\because M_4$ has lower V_{sd} current)

But this argument can't be made $\therefore I$ in M_3, M_1 same as in M_2, M_4 so

$$\therefore V_{d_2} = V_{d_1}$$

Equivalent gm \Rightarrow

$$\frac{I_{out}}{V_{in}}$$

so if we calculate, $(gm)_{eq}$ Req \Rightarrow Gain not obtain

to find $\frac{I_{out}}{V_{in}}$ \Rightarrow Norton's [short circuit] \Rightarrow to make small signal short,

small signal \Rightarrow but no DC changes

\Rightarrow we can put V source at V_{d_2}


$$\Rightarrow \boxed{V = V_{d_2} = V_{d_1}}$$

g same D or

$M_4 > M_3$

current

Small signal of stage-1

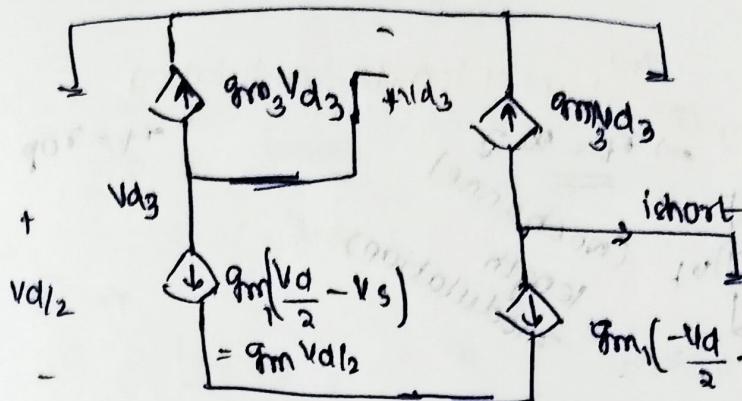

$$\boxed{Vd_3 = qm \left(\frac{Vd}{2} \right)}$$

KCL:


$$qm_3 Vd_3 + qm_1 \frac{Vd}{2} = 0$$

$$\boxed{Vd_3 = -\frac{qm_1 Vd}{2 qm_3}}$$

$$\Rightarrow 0 = \frac{Vd}{2} + \frac{-Vd_1}{2} \Rightarrow \frac{Vd + Vd_1}{2} = 0$$

$$\therefore Vd_1 = -Vd$$


same setup as
left one
in actual circuit

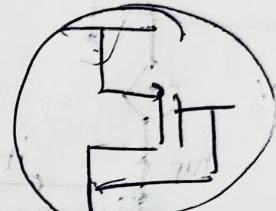

acts as
resistor
 $\frac{1}{qm_3}$

$$qm_3 Vd_3 = qm_3 \cdot \frac{qm_1}{2 qm_3} Vd \text{ of pair}$$
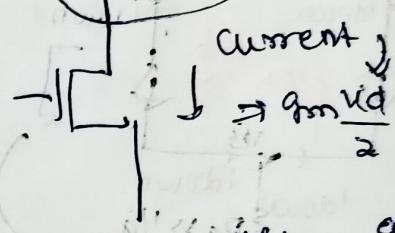
$$\text{Now } i_{\text{short}} = \frac{qm_1 Vd}{2} \quad (\text{KCL right side})$$




Current \downarrow

$$\Rightarrow -i_{d3} = qm_1 \frac{Vd}{2} \cdot \frac{1}{qm_3}$$

It is not only mirroring DC values but also ac mirroring.

$$\boxed{gm \text{ equivalent} = qm_3}$$

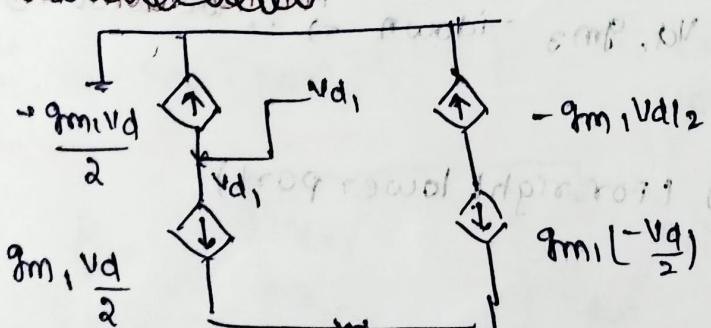

$V_s = 0$ (\because Current source is ideal)

so that's why we can

completely open current source so there is no path for $qm_1 \frac{Vd}{2}$, $qm_1 \frac{Vd}{2}$


$\therefore V_s = 0$ (KCL)

open

If τ_{ON} is also present $\Rightarrow \tau_t = \tau_{ON} || \tau_{op}$

When ① is not ideal, R_{ss} is present.

$$i_t = i_{up} + i_{down}$$

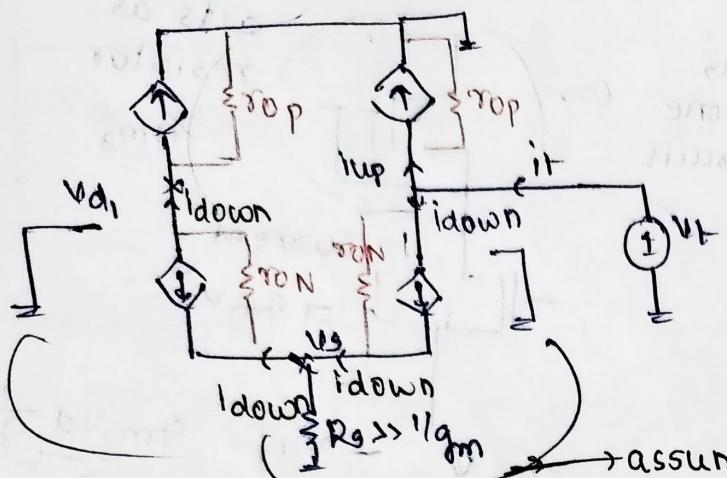

$$i_{\text{up}} \approx i_{\text{down}} + \frac{Vt}{r_{\text{op}}} \quad (1)$$

We know that the downward currents going to get mirrored

Crater is grounded (\therefore we are finding root).

$$Vd_1 = i_{\text{down}} \times \frac{1}{gm_3} \quad (\text{ignore } r_{\text{op}}) \quad \text{but } r_{\text{op}} > 1/gm_3$$

then right top corner current $\Rightarrow V_{dt}, g_m z = i_{down} \Rightarrow$ we wrote ①
in current source.

$$i_{\text{down}} = \frac{V_t - V_S}{R_{ON}} + g_m(-V_S) \quad (\text{KCL for right lower part})$$

$$i_{down} \tau_{ON} = V_t - V_S - g_m \tau_{ON} V_S$$

$$N_g(1+g_m \tau_{ON}) = N_t \text{ (down time due to switch off)} - g_m$$

$$\frac{\partial \sigma}{\partial t} = \text{transport}_S - \text{diffusion} - \text{idownron}$$

$$i_{down} = \frac{V_g - V_d}{R_{DN}} + q_m V_s \quad (\text{For Lower Left part})$$

$$i_{down} R_{DN} = V_g - V_d + R_{DN} q_m V_s$$

$$V_g (1 + q_m R_{DN}) = i_{down} R_{DN} + V_d,$$

$$V_g = \frac{i_{down} [R_{DN} + \frac{1}{q_m}]}{1 + q_m R_{DN}} = i_{down} \left[1 + \frac{1}{q_m R_{DN}} \right] + \frac{1}{q_m R_{DN}} + q_m V_s$$

$$V_g \approx \frac{i_{down}}{q_m} \quad (3)$$

sub in ② \Rightarrow

$$\frac{i_{down}}{q_m} = \frac{V_t - i_{down} R_{DN}}{1 + q_m R_{DN}}$$

$$V_t = i_{down} \left[\frac{1 + q_m R_{DN}}{q_m} + R_{DN} \right]$$

~~$$\frac{V_t}{i_t} = \frac{i_{down} \left[\frac{1 + q_m R_{DN}}{q_m} + R_{DN} \right]}{i_{down}}$$~~

ignore i_{down}

$$V_t = i_{down} \cdot R_{DN} \left[\frac{1}{R_{DN}} + \frac{q_m}{q_m} + 1 \right]$$

~~$$V_t = 2 i_{down} + \frac{V_t}{R_{top}}$$~~

$$V_t = i_{down} \cdot R_{DN} \cdot (2)$$

$$i_{down} = \frac{V_t}{2 R_{DN}}$$

① \Rightarrow

$$V_t = \frac{2 V_t}{2 R_{DN}} + \frac{V_t}{R_{top}}$$

$$\frac{V_t}{i_t} = (R_{DN} \parallel R_{top})$$

$$A_g = q_m (R_{DN} \parallel R_{top}) \quad (+ve) \quad (\text{Differential})$$

gain

skel at Vs Node